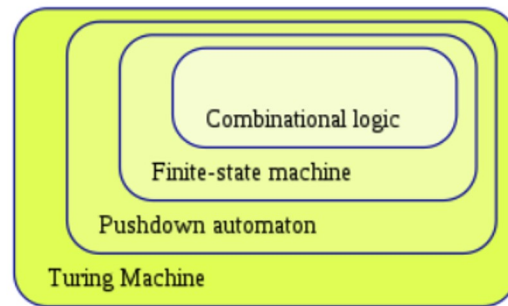


Lecture

- Last time:


- Boolean Algebra \Leftrightarrow Digital Circuits
 - Point: We can do a lot with just Combinational logic -- all true functions can be evaluated
 - Point: Digital Circuits can be built to evaluate all of these functions.
- All we need is And (*), Or (+) and Not (')
- Truth Table \rightarrow Boolean Algebra
- Boolean Algebra \rightarrow Circuits \rightarrow Boolean Algebra
- Minimization of Circuits
 - Algebraic Transformations:
 - Karnaugh Maps

- Today: More Combinational Circuits




Combinational Logic

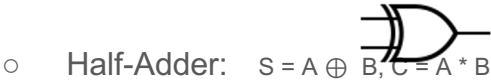
- Using just is tedious: AND (*), OR (+), NOT (')
- Solution: Build components and reuse!
 - XOR: $A \oplus B$ is equivalent to $(A + B) * (A' + B')$



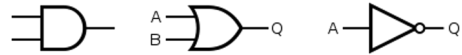- Bigger components and with more bits!
 - Binary Addition
 - Binary Subtraction
 - BCD Addition
 - Decoder
 - Multiplexer



XOR:

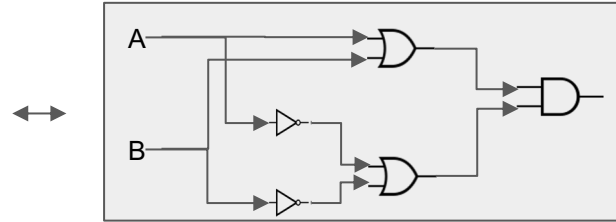


A	B	Carry	Sum
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

4-bit Bitwise AND

- $R = A \& B$

	1	0	1	1	A
&	0	1	1	0	B
	0	0	1	0	R

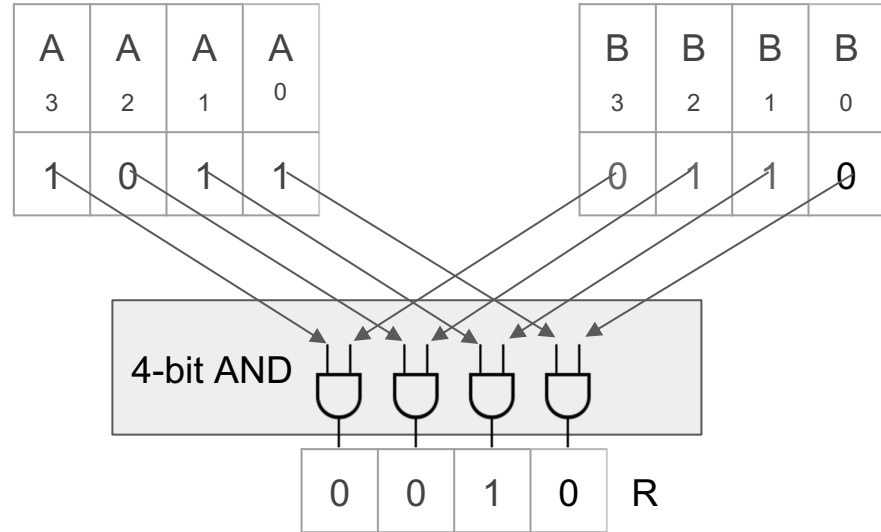- For a n-bit operation,
 - create n-duplicates of the base circuitry
 - layout duplicates in parallel
 - package it up




1-bit Binary Addition

- Recall:

- $A + B \rightarrow S, C$

			1	A
			1	B
+				
				S

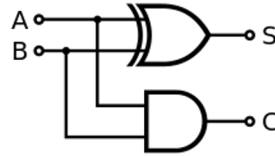

A	B	C _{out}	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

4-bit Binary Addition

- Recall:

- $C_{in} + A_x + B_x \rightarrow C_{out}, S_x$



	1	0	1	1
+	0	1	1	0

A

B


S

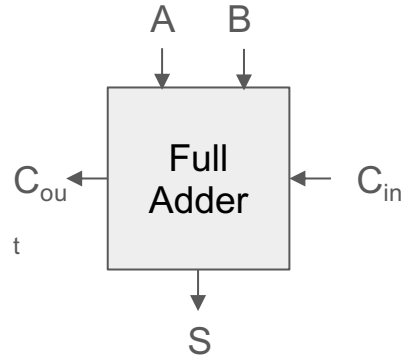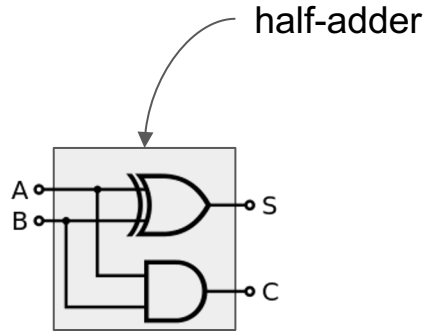- Half-Adder is not sufficient!
We need a Full-Adder



C_{in}	A	B	C_{out}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Full Adder

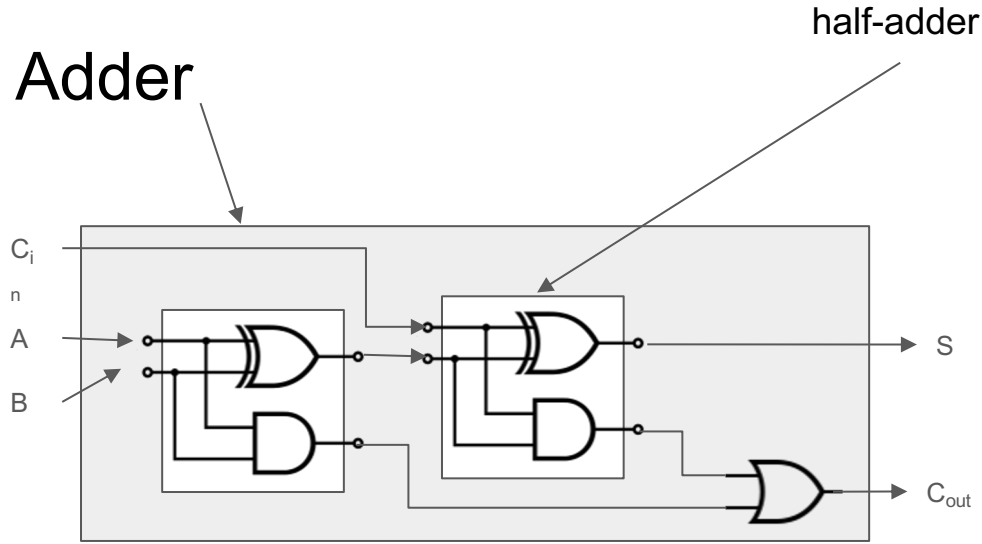


Got It? Any Questions

C_{in}	A	B	C_{out}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

- $C_{out} = AB + C_{in}(A \oplus B)$
- $S = C_{in} \oplus A \oplus B$

Full Adder

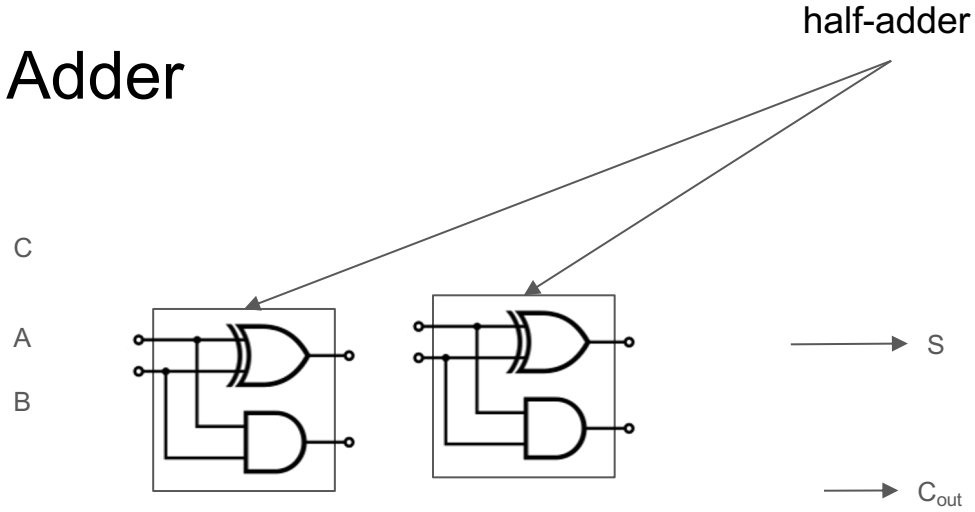


- $C_{out} = C'AB +$

Note: Renamed C_{in} to be C

C _{in}	A	B	C _{out}	S	
0	0	0	0	0	
0	0	1	0	1	
0	1	0	0	1	
0	1	1	1	0	C'AB
1	0	0	0	1	
1	0	1	1	0	
1	1	0	1	0	
1	1	1	1	1	

Use Sum of Products

Full Adder

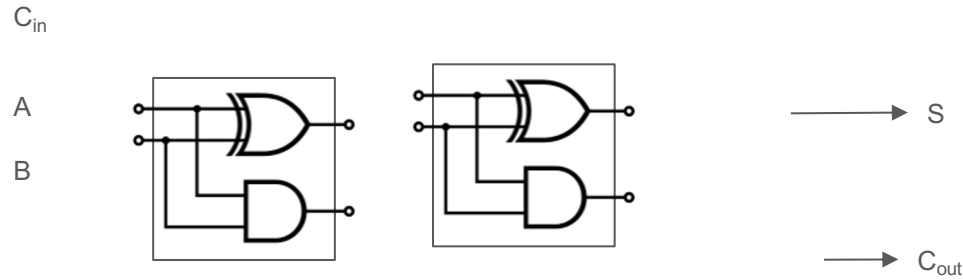


C_{in}	A	B	C_{out}	S	
0	0	0	0	0	
0	0	1	0	1	
0	1	0	0	1	
0	1	1	1	0	$C'AB$
1	0	0	0	1	
1	0	1	1	0	$CA'B$
1	1	0	1	0	CAB'
1	1	1	1	1	CAB

- $C_{out} = C'AB + CA'B + CAB' + CAB$

Use Sum of Products

Full Adder

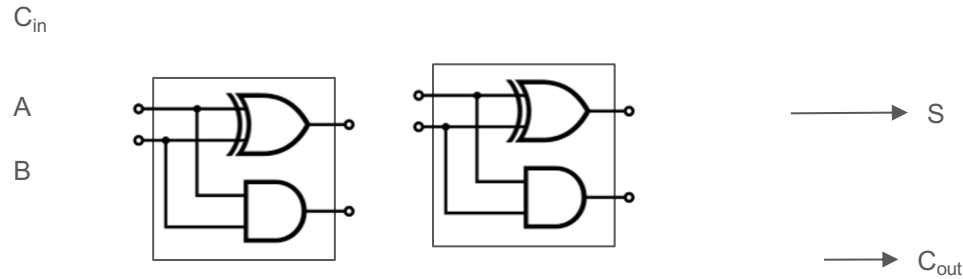


- $C_{out} = C'AB + CA'B + CAB' + CAB$
- $C_{out} = C'AB + CAB + CA'B + CAB'$

C_{in}	A	B	C_{out}	S	
0	0	0	0	0	
0	0	1	0	1	
0	1	0	0	1	
0	1	1	1	0	$C'AB$
1	0	0	0	1	
1	0	1	1	0	$CA'B$
1	1	0	1	0	CAB'
1	1	1	1	1	CAB

Use Commutative Property

Full Adder

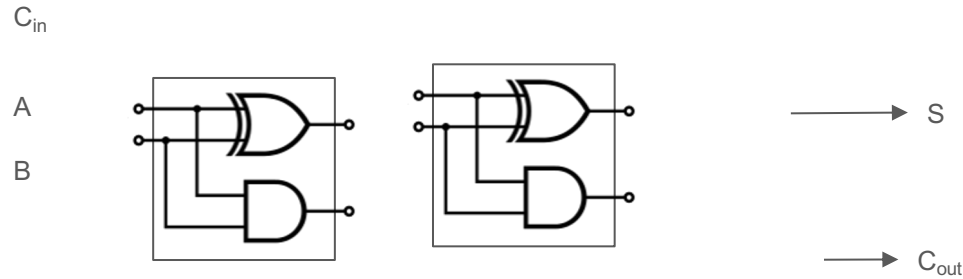


C_{in}	A	B	C_{out}	S	
0	0	0	0	0	
0	0	1	0	1	
0	1	0	0	1	
0	1	1	1	0	$C'AB$
1	0	0	0	1	
1	0	1	1	0	$CA'B$
1	1	0	1	0	CAB'
1	1	1	1	1	CAB

- $C_{out} = C'AB + CAB + CA'B + CAB'$
- $C_{out} = (C' + C)AB + CA'B + CAB'$

Use Distributive Property

Full Adder

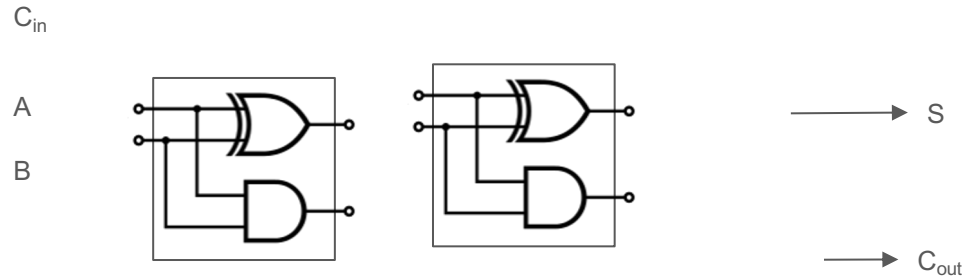


- $C_{out} = (C' + C)AB + CA'B + CAB'$
- $C_{out} = (\text{true})AB + CA'B + CAB'$

C_{in}	A	B	C_{out}	S	
0	0	0	0	0	
0	0	1	0	1	
0	1	0	0	1	
0	1	1	1	0	$C'AB$
1	0	0	0	1	
1	0	1	1	0	$CA'B$
1	1	0	1	0	CAB'
1	1	1	1	1	CAB

Use Complement Property

Full Adder

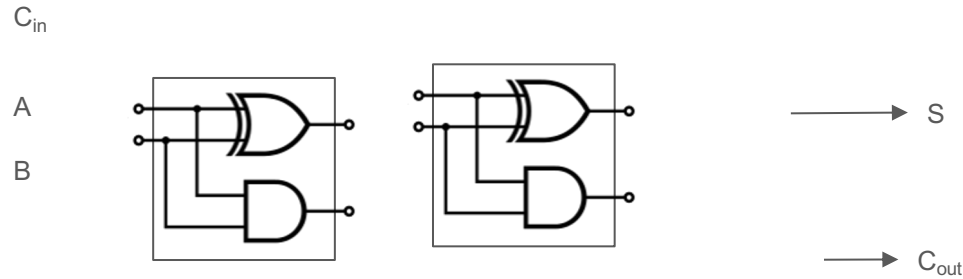


- $C_{out} = \boxed{(true)AB} + CA'B + CAB'$
- $C_{out} = AB + CA'B + CAB'$

C_{in}	A	B	C_{out}	S	
0	0	0	0	0	
0	0	1	0	1	
0	1	0	0	1	
0	1	1	1	0	$C'AB$
1	0	0	0	1	
1	0	1	1	0	$CA'B$
1	1	0	1	0	CAB'
1	1	1	1	1	CAB

Use Identity Property

Full Adder

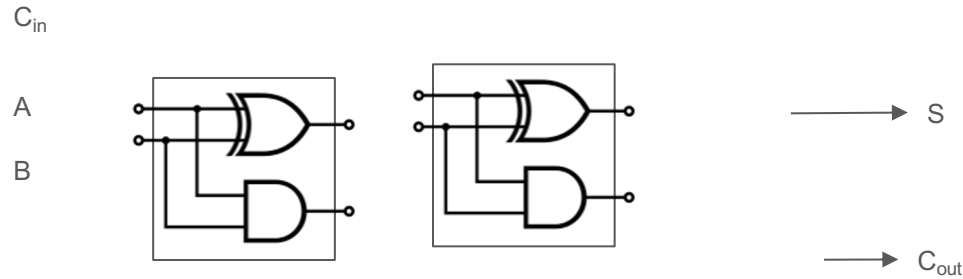


- $C_{out} = AB + CA'B + CAB'$
- $C_{out} = AB + C(A'B + AB')$

C_{in}	A	B	C_{out}	S	
0	0	0	0	0	
0	0	1	0	1	
0	1	0	0	1	
0	1	1	1	0	$C'AB$
1	0	0	0	1	
1	0	1	1	0	$CA'B$
1	1	0	1	0	CAB'
1	1	1	1	1	CAB

Use Distributive Property

Full Adder

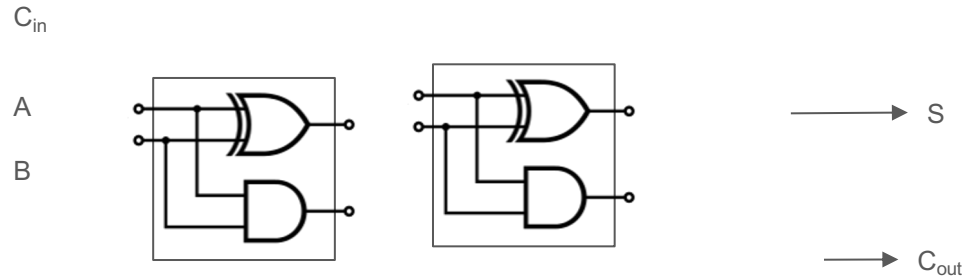


- $C_{out} = AB + C(A'B + AB')$
- ✓ $C_{out} = AB + C(A \oplus B)$

C_{in}	A	B	C_{out}	S	
0	0	0	0	0	
0	0	1	0	1	
0	1	0	0	1	
0	1	1	1	0	$C'AB$
1	0	0	0	1	
1	0	1	1	0	$CA'B$
1	1	0	1	0	CAB'
1	1	1	1	1	CAB

$$A \oplus B \Leftrightarrow A'B + AB'$$

Full Adder

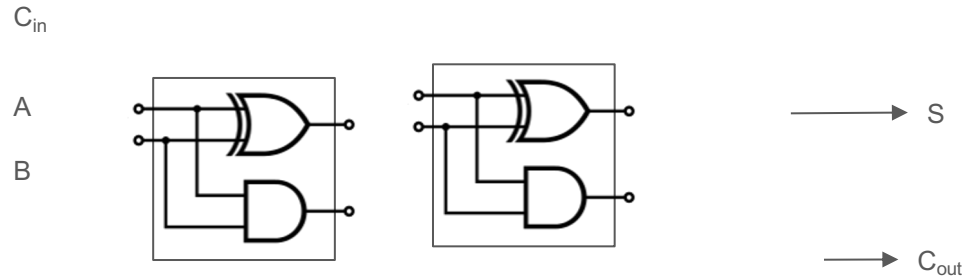

C	A	B	C_{out}	S	
0	0	0	0	0	
0	0	1	0	1	$C'A'B$
0	1	0	0	1	$C'AB'$
0	1	1	1	0	
1	0	0	0	1	$CA'B'$
1	0	1	1	0	
1	1	0	1	0	
1	1	1	1	1	CAB

Sum of Products:


$$C'A'B + C'AB' + CA'B' + CAB$$

✓ $C_{out} = AB + C(A \oplus B)$

● $S = C'A'B + C'AB' + CA'B' + CAB$

$$A \oplus B \Leftrightarrow A'B + AB'$$

Full Adder

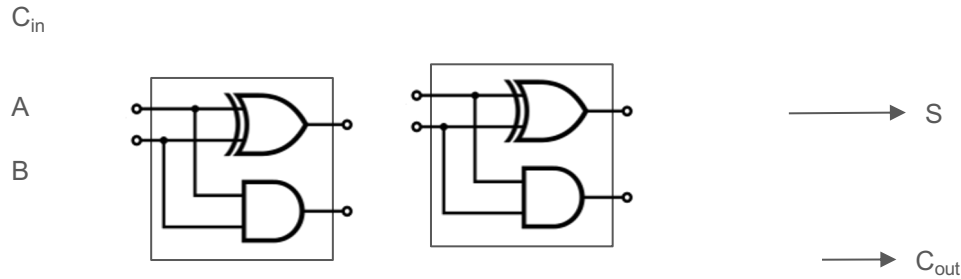

C	A	B	C_{out}	S	
0	0	0	0	0	
0	0	1	0	1	$C'A'B$
0	1	0	0	1	$C'AB'$
0	1	1	1	0	
1	0	0	0	1	$CA'B'$
1	0	1	1	0	
1	1	0	1	0	
1	1	1	1	1	CAB


- ✓ $C_{out} = AB + C(A \oplus B)$
- $S = C'A'B + C'AB' + CA'B' + CAB$
- ✓ $S = C \oplus A \oplus B$

Sum of Products:

$$\begin{aligned}
 & C'A'B + C'AB' + CA'B' + CAB \\
 &= C'(A'B + AB') + C(A'B' + AB) \\
 &= C'(A \oplus B) + C(A \oplus B)' \\
 &= C \oplus (A \oplus B)' \\
 &= C \oplus A \oplus B
 \end{aligned}$$

$$A \oplus B \Leftrightarrow A'B + AB'$$

Full Adder

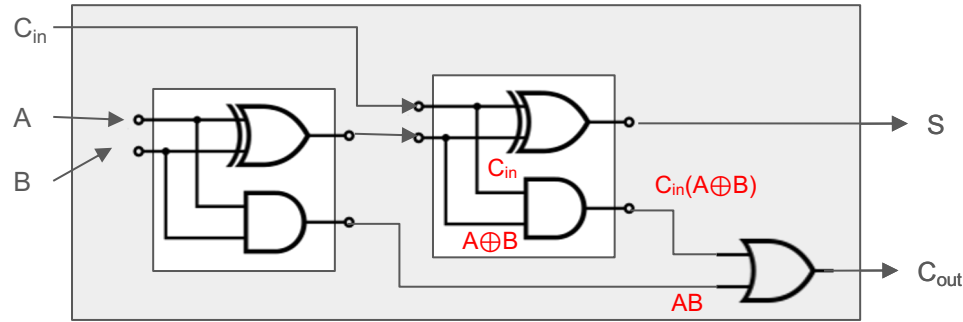

$$\checkmark \quad C_{out} = AB + C_{in}(A \oplus B)$$

$$\checkmark \quad S = C_{in} \oplus A \oplus B$$

C	A	B	C_{out}	S	
0	0	0	0	0	
0	0	1	0	1	
0	1	0	0	1	
0	1	1	1	0	
1	0	0	0	1	
1	0	1	1	0	
1	1	0	1	0	
1	1	1	1	1	


Note: Renamed C to be C_{in}

4-bit Binary Addition

(aka: 4-bit Full Adder)

	1	0	1	1
+	0	1	1	0

A
B
S

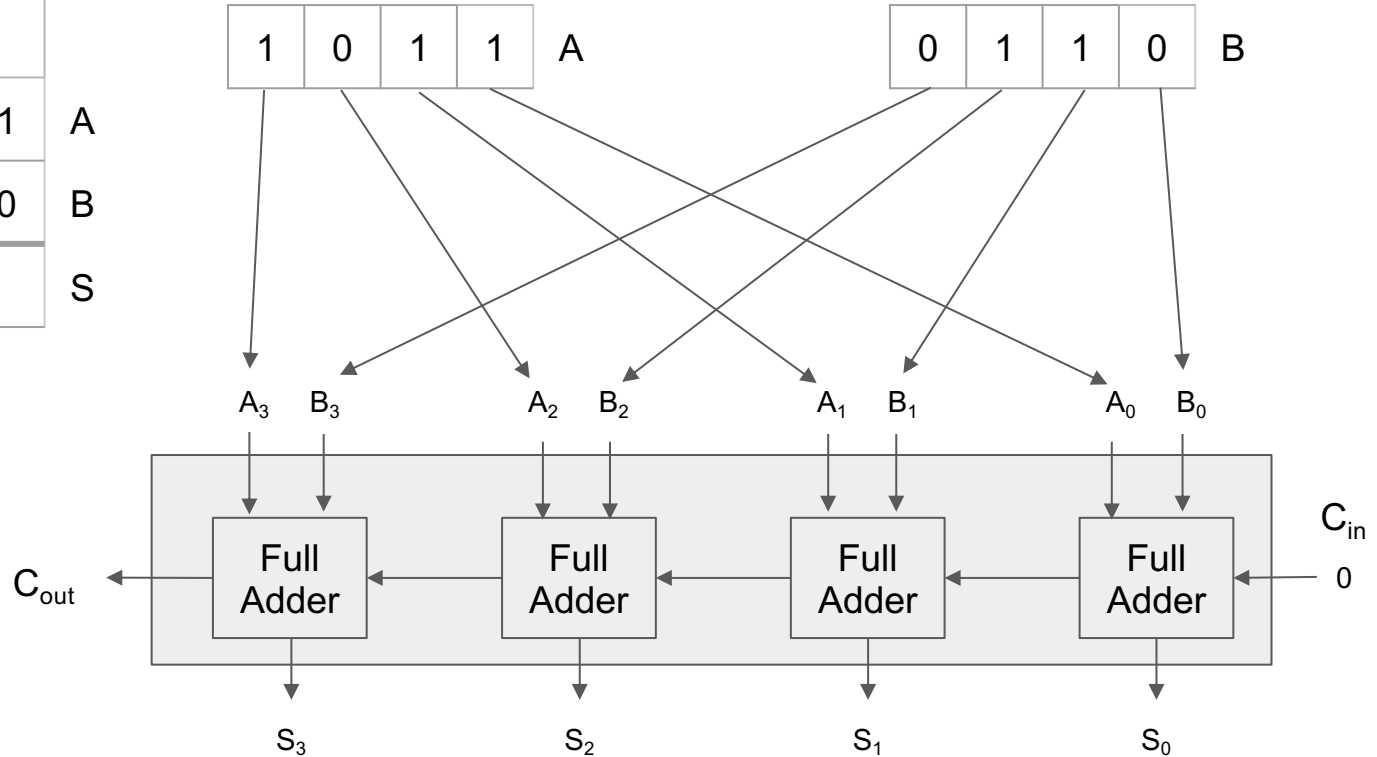


Binary Subtractor


- Recall: $A - B$

- $= A + (2\text{'s complement of } B)$

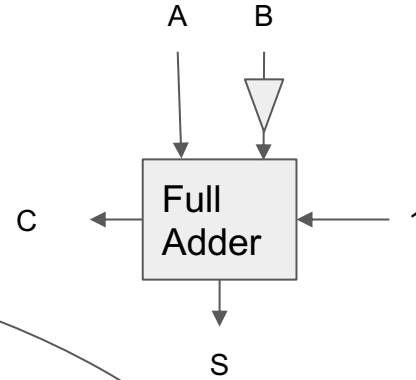- $= A + (1\text{'s complement of } B) + 1$



- 4-bit Binary Subtractor

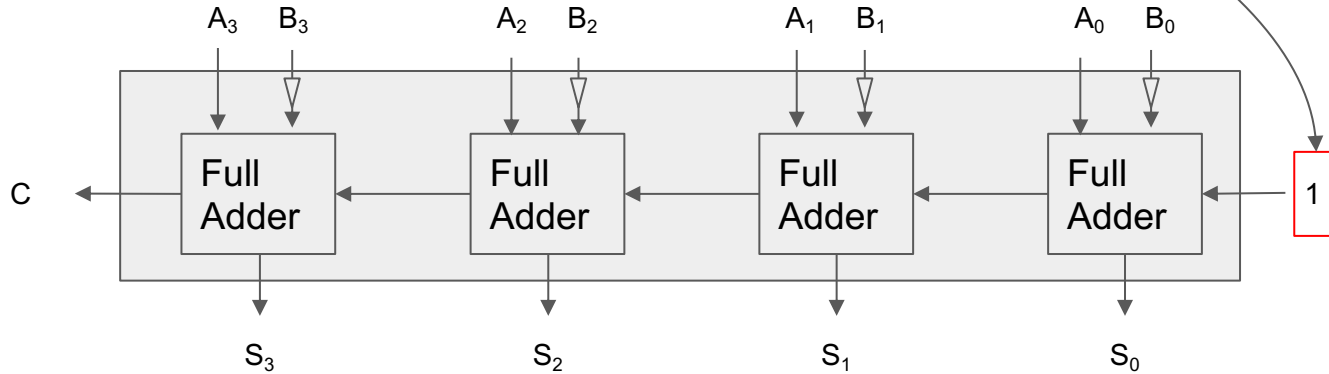

4-bit BCD Addition

- BCD: 35 + 28

35
+ 28

	0	1	1	1			0	0	0	0					
	0	0	1	1	3		0	1	0	1	5				
+	0	0	1	0	2	+	1	0	0	0	8				

#	Encoding $S_3S_2S_1S_0$		Encoding $S_3S_2S_1S_0$
0	0 0 0 0	8	1 0 0 0
1	0 0 0 1	9	1 0 0 1
2	0 0 1 0	invalid	1 0 1 0
3	0 0 1 1		1 0 1 1
4	0 1 0 0		1 1 0 0
5	0 1 0 1		1 1 0 1
6	0 1 1 0		1 1 1 0
7	0 1 1 1		1 1 1 1

- Perform Regular Binary Addition, but account for the invalid patterns
- Add six upon whenever you are in the deadzone or there is overflow
 - Invalid = $S_3 * (S_2 + S_1)$
 - Overflow = C_{out}

4-bit BCD Addition

	0	1	1	0
+	0	1	0	1

6

5

	0	0	1	0
+	0	1	0	1

2

5

